

الجامعة الإسلامية العالمية ماليزيا

INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA

END OF SEMESTER EXAMINATION  
SEMESTER I, 2013/2014 SESSION

KULLIYAH OF ENGINEERING

Programme : ENGINEERING Level of Study : UG 1  
Time : 2:30 pm-5:30 pm Date : 28/12/2013  
Duration : 3 Hrs  
Course Code : ECE 1311 Section(s) : ALL  
Course Title : **Electric Circuits**

This Question Paper Consists of **Five (5)** Printed Pages (Including Cover and a blank page) with **Five (5)** Questions.

**INSTRUCTION(S) TO CANDIDATES**

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- A total mark of this examination is **100**.
- This examination is worth **50%** of the total assessment.
- Answer **ALL FIVE (5)** questions.

**Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.**

**Q.1 [20 marks]**

- (a) The current,  $i(t)$ , passing through an element is shown in Fig. 1(a). Determine the total charge that passed through the element at  $t = 1s, 3s$  and  $5s$ .

(10 marks)

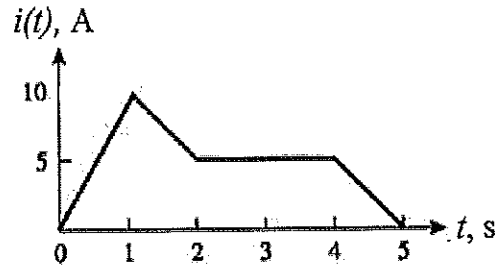


Fig. 1(a)

- (b) Find  $V_o$  in the two-way power divider circuit in Fig. 1(b).

(10 marks)

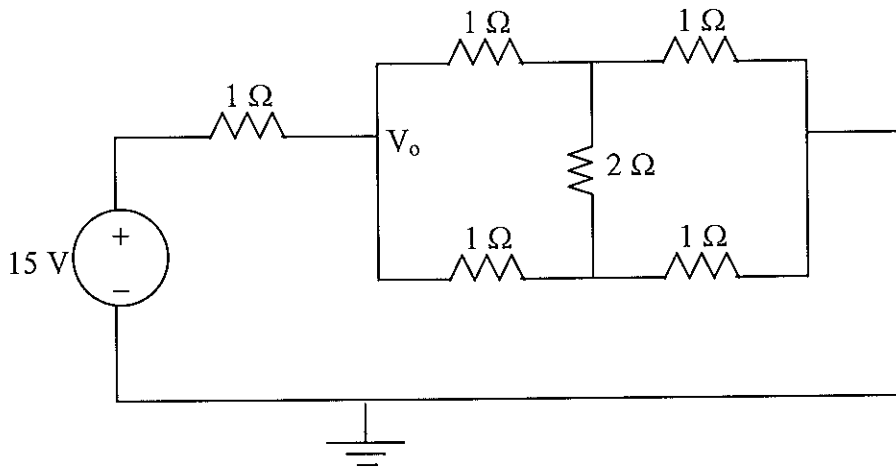


Fig. 1(b)

**Q.2 [20 marks]**

- a) Obtain the node-voltage equations for the circuit in Fig 2(a) by inspection. Then solve for  $V_o$ .

(12 marks)

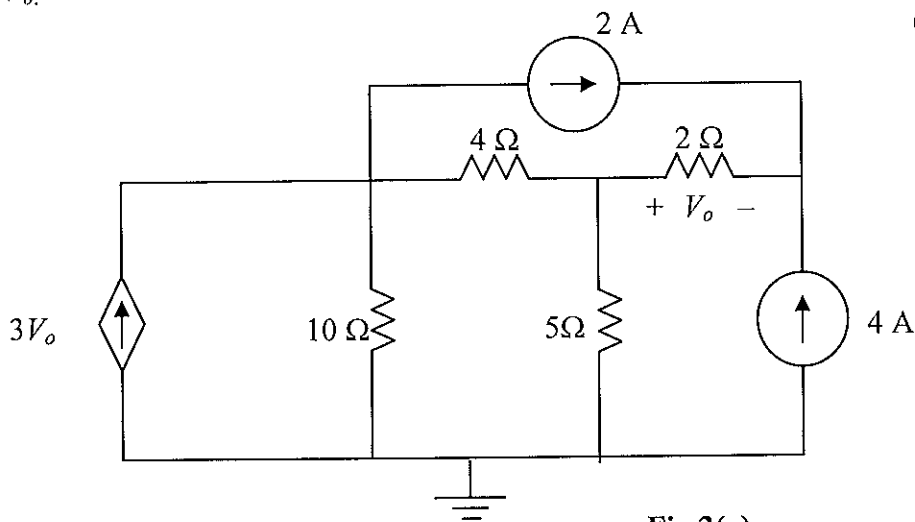


Fig 2(a)

b) Use source transformation to find  $V_o$  in the circuit of Fig 2(b).

(8 marks)

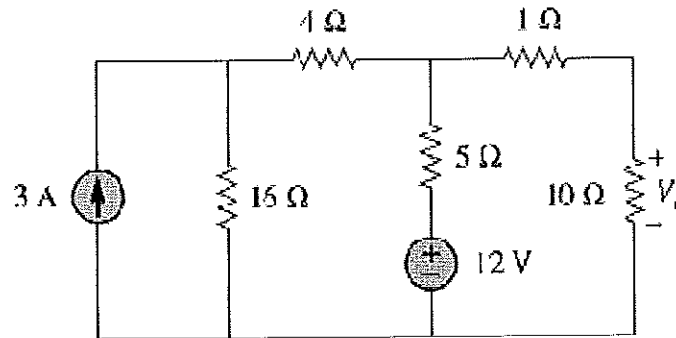


Fig 2(b)

**Q.3 [20 marks]**

(a) For the circuit in Fig. 3 (a), determine:

- i. the voltage across each capacitor
- ii. energy stored in each capacitor

(5 marks)

(5 marks)

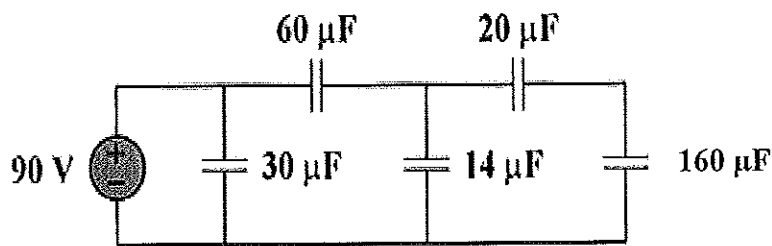


Fig. 3(a)

(b) Find the equivalent impedance of the circuit in Fig. 3(b).

(10 marks)


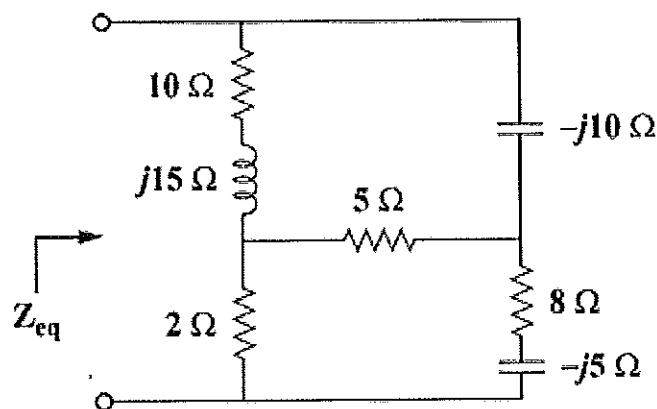


Fig. 3(b)


**Q.4 [20 marks]**

- a) Using the circuit of **Fig 4(a)**, determine the mesh currents  $i_1$  and  $i_2$ . Let  $v_1 = 10 \cos 4t$  V and  $v_2 = 20 \cos(4t - 30^\circ)$  V. **(10 marks)**

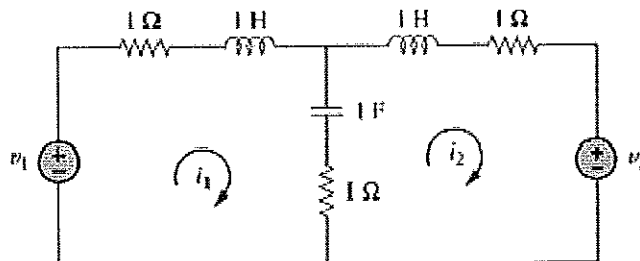

**Fig 4(a)**


- b) Use superposition principle to obtain  $v_x$  in the circuit of **Fig 4(b)**. Let  $v_s = 50 \sin 2t$  V and  $i_x = 12 \cos(6t + 10^\circ)$  A. **(10 marks)**

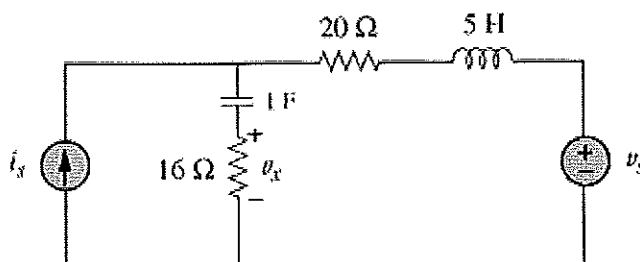

**Fig 4(b)**

**Q.5 [20 marks]**


- a) Find the Thevenin and Norton equivalent circuits at terminals a-b of the circuit in **Fig. 5(a)**. Then, assuming that the load impedance is to be purely resistive, what load should be connected to terminals a-b of the circuits in **Fig. 5(a)** so that the maximum power is transferred to the load?

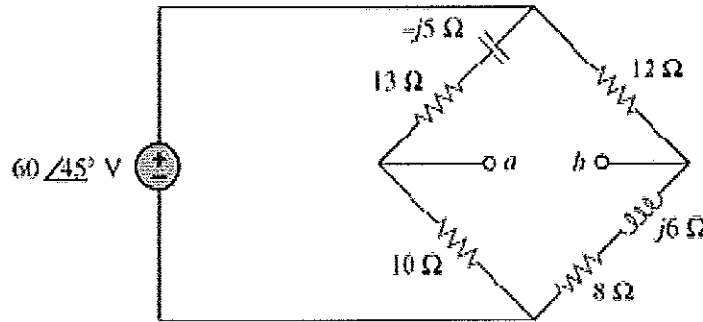

**Fig. 5(a)**

- b) Referring to the circuit in **Fig. 5(b)**, determine:

- i. the power factor
- ii. the average power delivered by the source
- iii. the reactive power
- iv. the apparent power
- v. the complex power

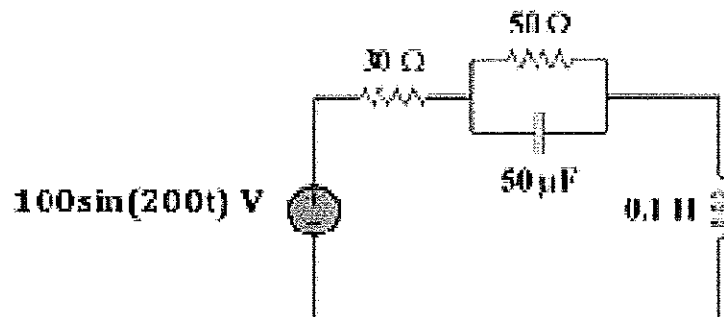

**Fig. 5(b)**