



الجامعة الإسلامية العالمية ماليزيا

INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA

**END OF SEMESTER EXAMINATION  
SEMESTER I, 2012/2013 SESSION  
KULLIYAH OF ENGINEERING**

Programme : Engineering Level of Study: UG 1

Time : 2:30p.m.-5:30p.m. Date : 29/12/2012

Duration : 3Hrs

Course Code : ECE 1311 Section(s) : ALL

Course Title : **Electric Circuits**

This question paper consists of six (6) printed pages (including a coverpage) with five (5) questions.

**INSTRUCTION(S) TO CANDIDATES**

**DO NOT OPEN UNTIL YOU ARE INSTRUCTED TO DO SO**

- You are required to write down all your working steps in a clear manner.
- Write your answers in the answer sheet provided.
- The total mark for this examination is 100.
- This examination is worth 50% of the total assessment.
- You may use 2B pencil or any pencil of equivalent shades of grey for drawing or sketching purposes.
- Answer **ALL QUESTIONS**.

**Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal.**

**Q.1 [20 marks]**

(a)

i. Find the current  $i(t)$  flowing through a device if the charge flow is given by

$$q(t) = 5 \sin 40t \text{ C} \quad (3 \text{ marks})$$

ii. The current flowing through an element is shown in Fig. 1(a). Determine the total charge flowing through the element at  $t = 10 \text{ ms}$ . (5 marks)

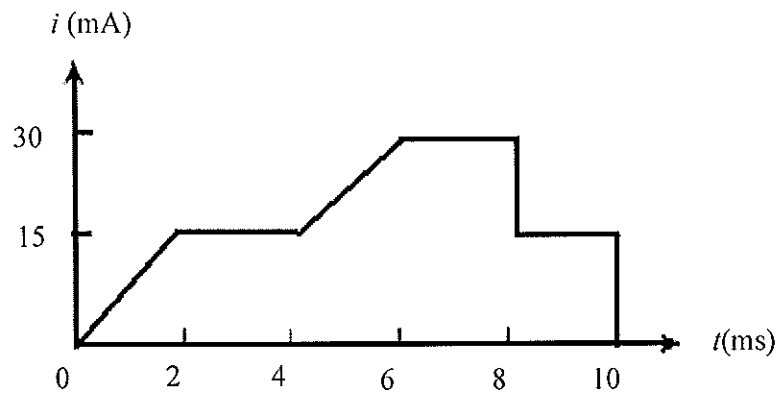


Fig. 1(a)

(b) Consider a circuit shown in Fig. 1(b).

- i. Find the equivalent resistance and conductance seen by the source. (4 marks)
- ii. Find the overall total dissipated power. (3 marks)
- iii. Find  $i_1$  and  $v_1$  using current division rule and voltage division rule respectively. (5 marks)

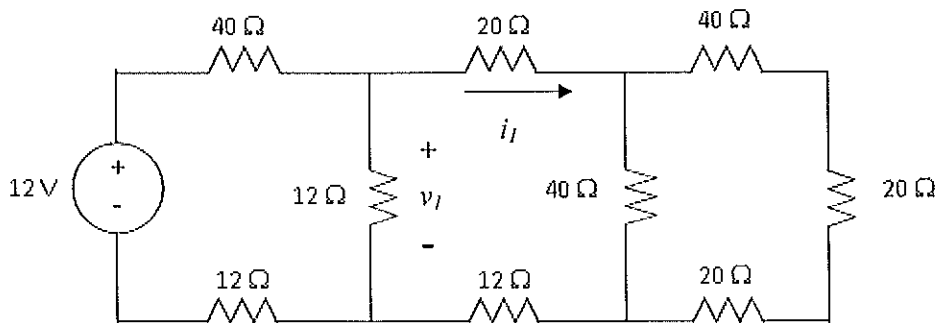


Fig. 1(b)

**Q.2 [20 marks]**

- (a) Use mesh analysis to determine  $i_1$ ,  $i_2$  and  $i_3$  for the circuit in Fig. 2(a). (8 marks)

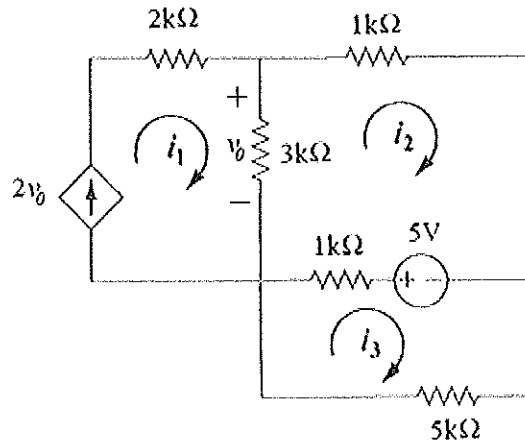


Fig. 2(a)

- (b) Use nodal analysis to calculate the voltage across the  $2\Omega$  resistor for the circuit in Fig. 2(b). (12 marks)

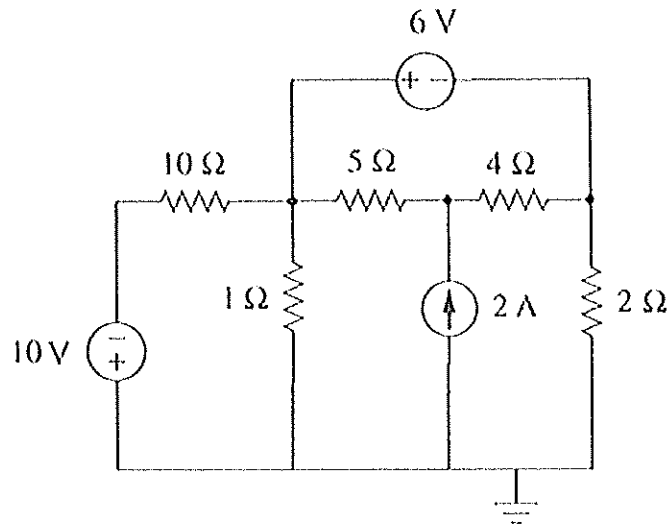


Fig. 2(b)

## Q.3 [20 marks]

- (a) Use superposition principle to find  $v_x$  in the circuit of Fig. 3(a). (8 marks)

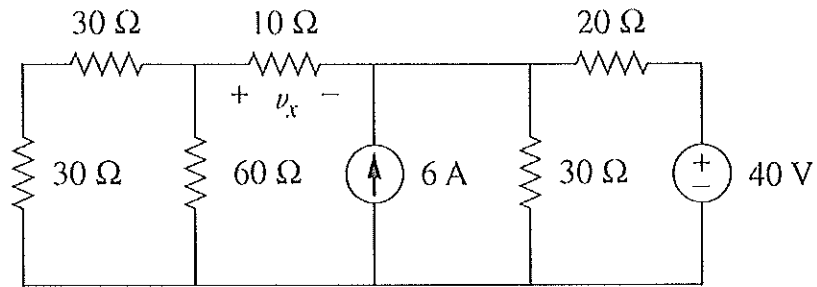


Fig. 3(a)

- (b) For the circuit in Fig. 3(b), determine the Norton's equivalent at terminals a-b. Then, (i) find  $R_L$  for maximum power deliverable to  $R_L$  and (ii) determine the maximum power. (12 marks)


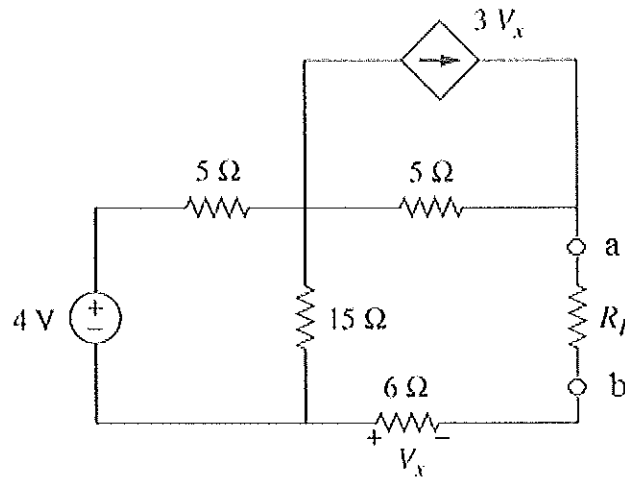


Fig. 3(b)


**Q.4 [20 marks]**

- (a) Draw the circuit shown in Fig. 4(a) under DC conditions. Find out the voltage across the capacitor and the current through the inductor. Also, find the energy stored in the inductor and the capacitor. **(8 marks)**

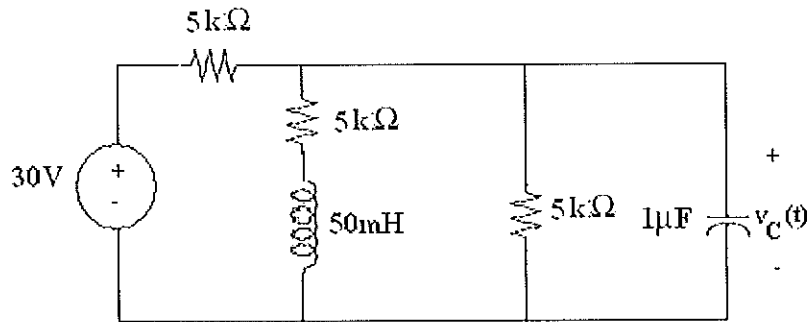

**Fig. 4(a)**

- (b) Find the input impedance,  $Z_{in}$ , of the circuit shown in Fig. 4(b). Calculate the input current  $I$  and  $I_1$  if  $V_s = 50\cos(\omega t + 60^\circ)$  V, and find the phase difference between the two currents. **(12 marks)**

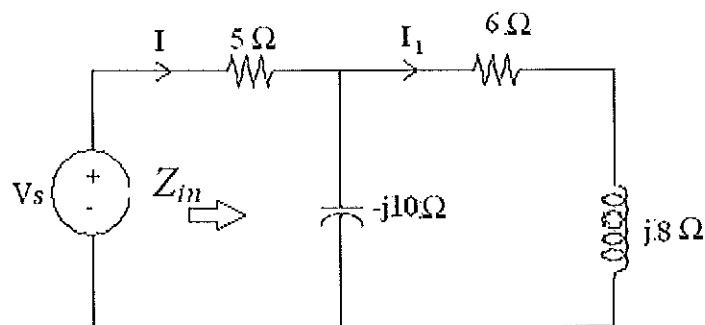

**Fig. 4(b)**

## Q.5 [20 marks]

- (a) Use source transformation to find  $V$  in Fig. 5(a) if  $v_1(t) = 120 \cos(\omega t - 15^\circ)V$ ,  $i(t) = 6 \sin(\omega t + 30^\circ)A$ , and  $\omega = 100 \text{ rads}^{-1}$ . (8 marks)

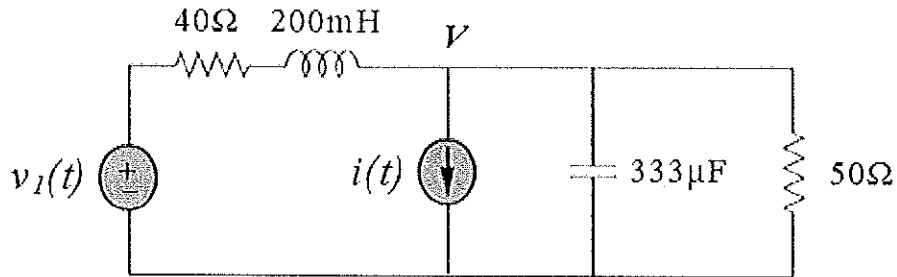


Fig. 5(a)

- (b) For the circuit in Fig. 5(b), obtain:

- i. The complex power and apparent power of the source. (6 marks)
- ii. The real power and reactive power of the source. (4 marks)
- iii. The power factor of the source and specify whether it is leading or lagging. (2 marks)

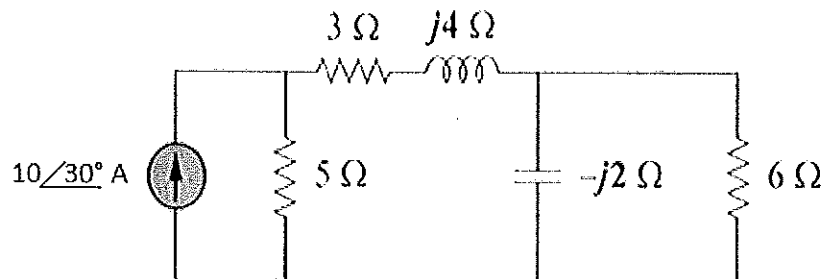


Fig. 5(b)