



الجامعة الإسلامية العالمية ماليزيا

INTERNATIONAL ISLAMIC UNIVERSITY MALAYSIA

END-OF-SEMESTER EXAMINATION

SEMESTER II, 2013/2014 SESSION

KULLIYAH OF ENGINEERING

Programme : Engineering

Level of Study : UG 1

Time : 02:30 – 05:30PM

Date : 28/05/2014

Duration : 3 Hour

Course Code : ECE 1311

Section(s) : All

Course Title : **Electric Circuits**

This Question Paper Consists of **FIVE (5)** Printed Pages (Including Cover Page) with **FIVE (5)** Questions.

INSTRUCTION(S) TO CANDIDATES

DO NOT OPEN UNTIL YOU ARE ASKED TO DO SO

- Total mark of this examination is **100**.
- This examination is worth **50%** of the total assessment.
- Answer all **FIVE (5)** questions. All questions carry equal marks.

Any form of cheating or attempt to cheat is a serious offence which may lead to dismissal

Question 1 [20 marks]

- (a) The current flowing distribution through a device over 12 seconds of time is as shown in Fig. 1a. Find the charge flowing through the device over the interval 0-12 seconds.

(4 marks)

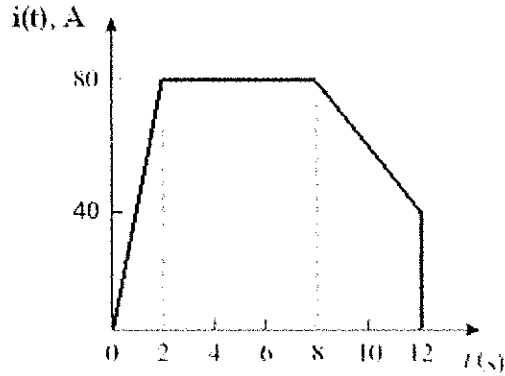


Fig. 1(a)

- (b) Find the energy consumed by the device over a period of 12 hours, assuming its power rating is as shown in Fig. 1(b).

(4 marks)

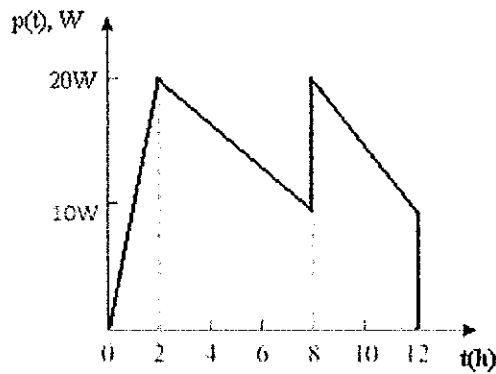


Fig. 1(b)

- (c) Use current division to find the current i_x in the circuit shown in Fig. 1(c). **(6 marks)**

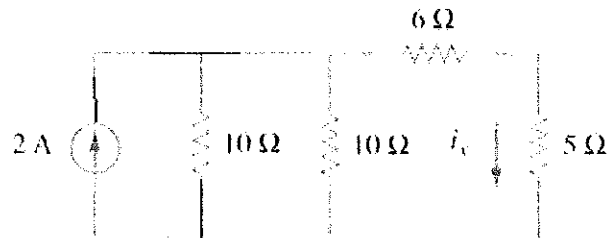


Fig. 1(c)

(d) Use voltage division to find the voltage V_x in the circuit shown in Fig. 1 (d). (6 marks)

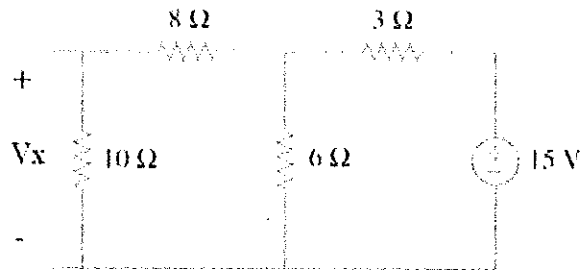


Fig. 1(d)

Question 2 [20 marks]

(a) Use nodal analysis to find v_1 , v_2 and v_3 in the circuit of Fig. 2(a). (10 marks)

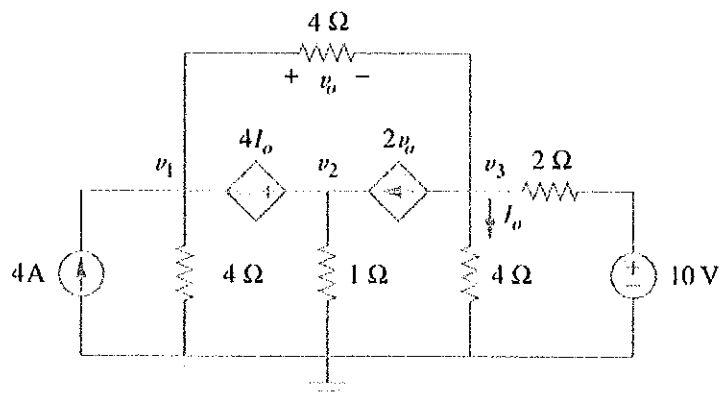


Fig. 2(a)

(b) Find and draw the Thevenin's and Norton's equivalents looking into terminals $a-b$ of the circuit shown in Fig. 2(b). What value of the resistor connected across terminals $a-b$ will absorb maximum power from the circuit? Also determine the maximum power. (10 marks)

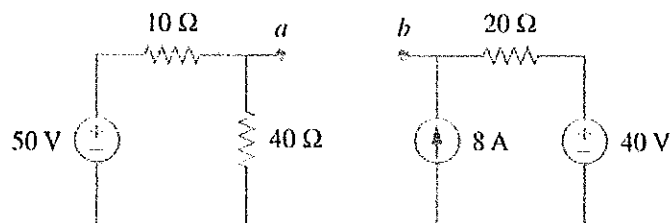


Fig. 2(b)

Question 3 [20 marks]

- (a) Find v_C , i_L , and the energy stored in the capacitor and inductor in the circuit of Fig. 3(a) under dc, steady-state conditions. (10 marks)

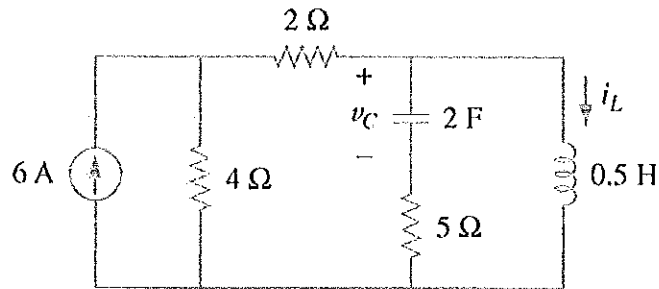


Fig. 3(a)

- (b) For the following pairs of sinusoids, determine which one leads and by how much? (5 marks)

$$v_1(t) = 50 \cos(112t + 10^\circ) \text{ and } v_2(t) = -20 \cos 112t$$

- (c) A parallel RLC circuit has the node equation

$$\frac{dv}{dt} + 50v + 100 \int v dt = 110 \cos(377t - 10^\circ)$$

Determine $v(t)$. You may assume that the value of the integral at $t = -\infty$ is zero.

(5 marks)

Question 4 [20 marks]

- (a) In the circuit of Fig. 4(a), find equivalent impedance (Z_{eq}) at the terminals a-b. Assume $\omega = 20$ rad/s. (10 marks)

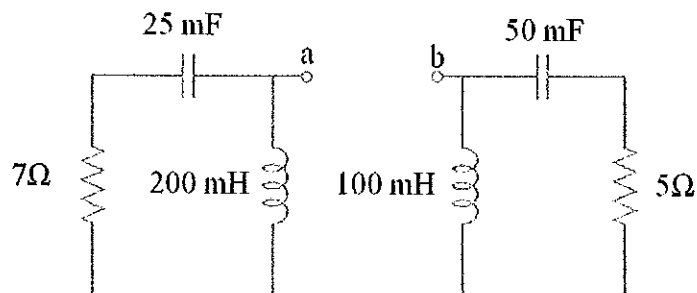


Fig. 4(a)

(b) Using mesh analysis, find I_1 and I_2 in the circuit of Fig. 4(b).

(10 marks)

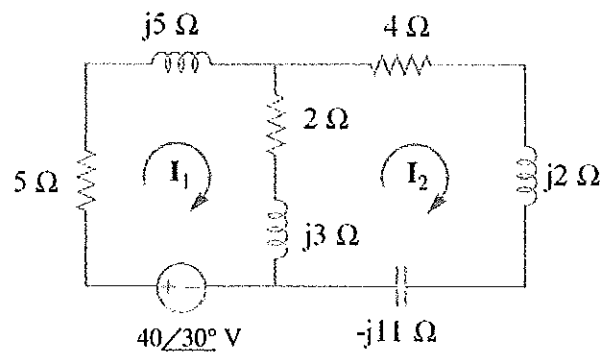


Fig. 4(b)

Question 5 [20 marks]

(a) Determine v_o in the circuit of Fig. 5a using superposition.

(10 marks)

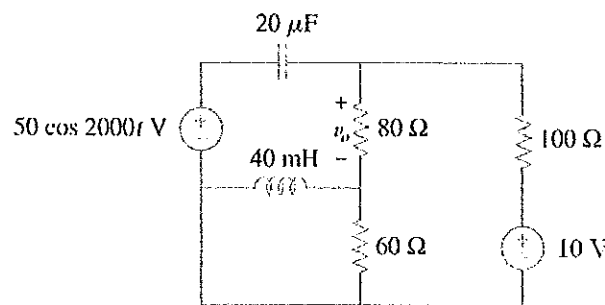


Fig. 5(a)

(b) For the circuit of Fig. 5(b), calculate:

(10 marks)

- i. The power factor. State whether it is leading or lagging.
- ii. The average power delivered by the source
- iii. The reactive power
- iv. The apparent power
- v. The complex power

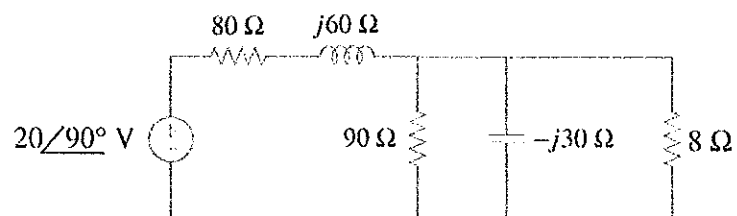


Fig. 5(b)